

## Voltage division with a potentiometer

### Aim of the experiment

- Investigation of a simple voltage divider
- Investigation of a loaded voltage divider
- Setup of a voltage divider with potentiometer

### Foundations

Kirchhoff's voltage law states that the sum of all voltages in a closed loop is equal to zero.


With a voltage divider it is possible to divide up voltages and in particular tap lower partial voltages. A voltage divider generally consists of two resistors, between which the applied  $U$  is divided into two partial voltages (voltage drops). Voltage dividers are used for example in measuring probes or to set operating points (voltage conditions) for active components, e.g. with a transistor/amplifier circuit.

In an initial test a voltage divider is created from various resistors and the output voltages in particular are measured. In a second test the loaded voltage divider is tested. Finally, a voltage divider with a potentiometer is set up and the output voltage is measured.

### Devices

1 plug-in board, DIN A4 .....	576 74
1 set 10 bridging plugs .....	501 48
1 STE resistor 47 $\Omega$ .....	577 28
2 STE resistor 100 $\Omega$ .....	577 32
1 STE resistor 150 $\Omega$ , .....	577 34
1 STE resistor 470 $\Omega$ .....	577 40
1 STE potentiometer 220 $\Omega$ .....	577 90
1 DC power supply, 0... $\pm$ 15 V .....	521 45
2 multimeter LD analog 20 .....	531 120
3 pairs of cables, 50 cm, red and blue .....	501 45

Fig. 1: Simple voltage divider

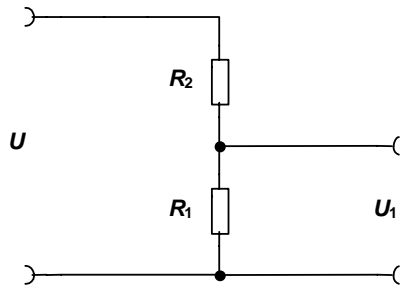


With non-loaded voltage dividers the current strength  $I$  results from the applied voltage  $U$  and the sum of the resistors  $R_1$  und  $R_2$ :

$$I = \frac{U}{R_1 + R_2} \quad (1)$$

and thereby for the voltage drop, e.g. at resistor  $R_1$

$$U_1 = I \cdot R_1 = U \cdot \frac{R_1}{R_1 + R_2} \quad (2)$$

Fig. 2: Loaded voltage divider

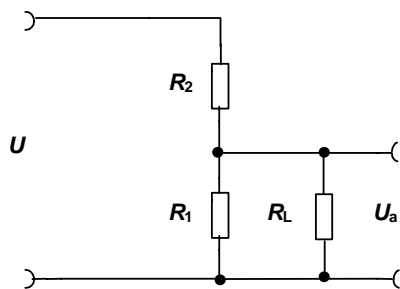

With a loaded voltage divider a current additionally flows via a load resistor  $R_L$ . This results in the current strength  $I$  increasing along with the voltage drop across resistor  $R_2$  and thereby a drop in the output voltage  $U_a$ .

The following applies to resistor  $R_1^*$  (parallel connection of  $R_1$  and  $R_L$ ):

$$R_1^* = \frac{R_1 \cdot R_L}{R_1 + R_L} \quad (3)$$

and thereby to the current strength:

$$I = \frac{U}{R_2 + \frac{R_1 \cdot R_L}{R_1 + R_L}} \quad (4)$$


and for the voltage taken per (2):

$$U_a = U \cdot \frac{R_1^*}{R_1^* + R_2} \quad (5)$$

or

$$U_a = U \cdot \frac{R_1}{R_1 + R_2 + \frac{R_1 \cdot R_2}{R_L}} \quad (6)$$

Fig. 3: Voltage divider with potentiometer

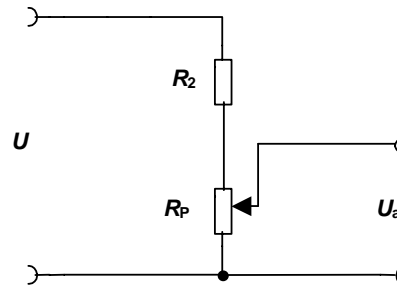

With a potentiometer with a resistor  $R_P$  the voltage drop per (2) is

$$U_P = U \cdot \frac{R_P}{R_P + R_2} \quad (7)$$

This allows an accordant adjustment of the voltage  $U_a$  between 0 V and  $U_P$  via the respective component resistor.

The resistor  $R_2$  serves here as a series resistor, so that no short circuit can be set.

### Apparatus and method

*Note:* Observe the measurement quantities and polarities at the measuring devices with all tests.

#### a) Simple voltage divider

- Set up test in accordance with Fig. 1 with  $R_2 = 100 \Omega$ . First apply no resistance for  $R_1$  (i.e.  $R_1 = \infty$ ).
- Set voltage  $U$  at the power supply to 15 V.
- Measure the current strength  $I$  and voltage  $U_1$  and note these in Table 1.
- Set the resistances  $R_1$  per Table and repeat the measurement each time.

#### b) Loaded voltage divider

- Set up test in accordance with Fig. 2 with  $R_1 = 470 \Omega$  and  $R_2 = 100 \Omega$ . First apply no resistance to resistor  $R_L$  (i.e.  $R_L = \infty$ ).
- Set voltage  $U$  at the power supply to 15 V.
- Measure the current strength  $I_L$  and voltage  $U_a$  and note these in Table 2.
- Set the load resistances  $R_L$  per Table 2 and repeat the measurement each time.

#### c) Voltage divider with potentiometer

- Set up the test per Fig. 3. First insert a bridging plug for resistor  $R_2$  (i.e.  $R_2 = 0 \Omega$ )
- Set voltage  $U$  at the power supply to 15 V.
- Actuate the potentiometer and observe voltage  $U_a$ . Measure the minimum and maximum voltage  $U_a$  each time and note these in Table 3.
- Set the (series) resistances  $R_2$  per Table 3 and repeat the measurement each time.

**Measurement examples and evaluation**


**a) Simple voltage divider**

Tab. 1: Single voltage divider ( $R_2 = 100 \Omega$ )

Measured values			$\frac{U_1}{V}$ calculated with:	
$\frac{R_1}{\Omega}$	$\frac{I}{mA}$	$\frac{U_1}{V}$	$R_1 \cdot I$	$U \cdot \frac{R_1}{R_1 + R_2}$
$\infty$	0	15.0	0	15*
150	60	9.0	9.0	9.0
100	73	7.6	7.3	7.5
47	100	4.7	4.7	4.8
0	150	0	0	0

(\* through limit value evaluation)

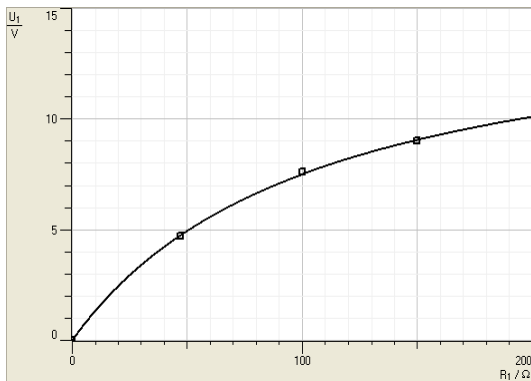- Calculate voltage  $U_1$  and enter in Table 1.
- Enter the partial voltage  $U_1$  in the graph against the resistance  $R_1$ :



- The output voltage  $U_1$  depends on the size of the resistance  $R_1$ .
- The greater the resistance  $R_1$  the greater the recorded voltage drop  $U_1$ .

**b) Loaded voltage divider**


Tab. 2: Loaded voltage divider ( $R_1 = 470 \Omega$  and  $R_2 = 100 \Omega$ )

Measured values			calculated with (4)	calculated with (6)
$\frac{R_L}{\Omega}$	$\frac{I}{mA}$	$\frac{U_a}{V}$	$\frac{I}{mA}$	$\frac{U_a}{V}$
$\infty$	27	12.5	26*	12.4
150	71	7.9	70	8.0
100	83	6.7	82	6.8
47	105	4.4	105	4.5
0	150	0	150	0*

(\* through limit value evaluation)

- The lower the load resistance, i.e. the more strongly the voltage divider is loaded, the lower the output voltage.

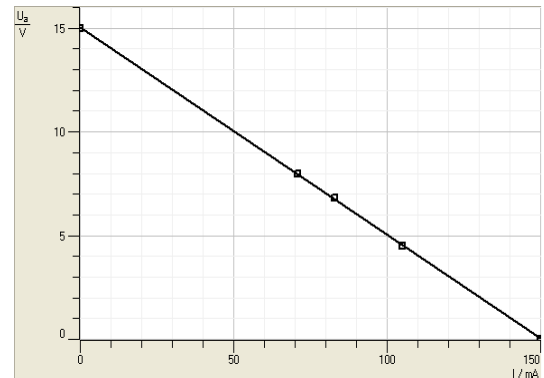- Enter the output voltage  $U_a$  in the graph against the current strength  $I_L$ :




- The output voltage  $U_a$  drops with the current strength  $I_L$ .
- The maximum current strength is limited to 150 mA by the series resistor  $R_2$ .

**c) Voltage divider with potentiometer**

Tab. 3: Voltage divider with potentiometer  $R_P = 220 \Omega$

$\frac{R_2}{\Omega}$	$\frac{U_{a,min}}{V}$	$\frac{U_{a,max}}{V}$	$\frac{U \cdot R_P}{R_P + R_2}$
0	0	15.0	15.0
47	0	12.2	12.4
150	0	8.6	8.9
470	0	4.8	4.8

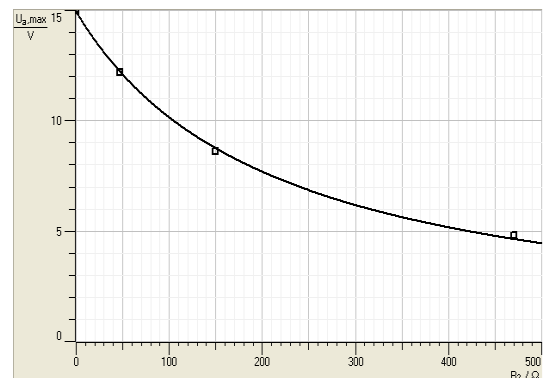- Calculate voltage  $U_P$  and enter in Table 3.
- It is possible to set an infinitely variable >output voltage from 0 V to a max.  $U_P$  with the potentiometer.
- Enter the max. output voltage  $U_{a,max}$  in the graph against the resistor  $R_2$ :



- The greater the (series) resistance  $R_2$  the lower the maximum recorded voltage drop  $U_{a,max}$ .

