

The field-effect transistor as an amplifier

Experiment Objectives

- Learning about the setup of the field-effect transistor's basic circuits.
- Determining amplification factors.

Basic Information

As a field-effect, an electric field's action is denoted on electric load carriers. This effect is used with so-called field-effect transistors (FET). Unlike bipolar transistors, these use only one type of load carrier, which is why they are also designated as unipolar transistors. The field-effect transistors' advantage is in their ability to operate or to control current with no load.

Unlike bipolar NPN or PNP transistors, the field-effect transistor needs no control current, only a control voltage. The control electrode G (gate) works like a capacitor with an electric field that cancels the load carrier from the line channel between the source S and the drain D or enhances it. The gate input (gate-source path) is therefore very highly resistive.

This study investigates the three basic circuits of the field-effect transistor as an amplifier. These field-effect transistor circuits correspond to bipolar transistors as follows:

Common source	–	Common emitter
Common drain	–	Common collector
Common gate	–	Common base

The voltage's, the amperage's and the power's amplification factors are calculated as follows:

$$V_U = \frac{U_A}{U_E} \quad V_I = \frac{I_A}{I_E} \quad V_P = \frac{P_A}{P_E} \quad (1)$$


Apparatus

1 Plug-in board DIN A4	576 74
1 Set of 10 bridging plugs	501 48
1 STE Transistor BF 244 (FET).....	578 77
1 STE Resistor 10 kΩ, 0.5 W	577 56
1 STE Resistor 15 kΩ, 0.5 W	577 58
1 STE Resistor 33 kΩ, 0.5 W	577 61
1 STE Resistor 68 kΩ, 0.5 W, 1 %	577 657
1 STE Resistor 100 kΩ, 0.5 W, 1 %	577 68
1 STE Resistor 1 MΩ, 0.5 W	577 76
2 STE Capacitors 1 μF, 100 V, 20 %	578 35
1 STE Capacitor 2.2 μF, 63 V, 20 %	578 36
1 STE Capacitor 47 μF, 40 V, 20 %	578 38
1 DC power supply 0...±15 V	521 45
1 Function generator S 12.....	522 621
1 Multimeter LDanalog 20	531 120
1 Two-channel oscilloscope 303	575 211
2 Screened cables BNC/4 mm	575 24
2 Pairs of cables, 50 cm, red and blue	501 45
1 Connecting lead, Ø 2,5 mm ² , 50 cm, black	501 28

Setup


Procedure

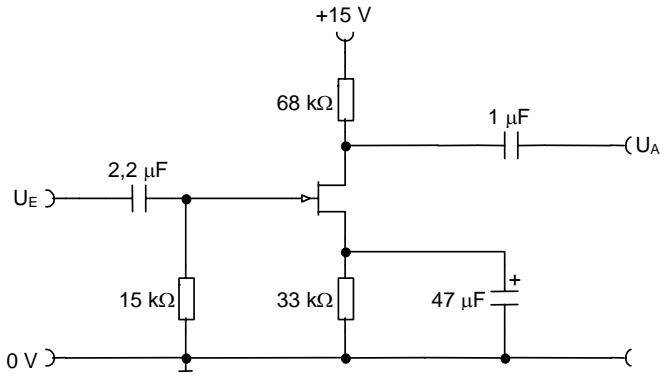a) Field-effect transistor in common source




- Experiment setup according to the illustration.
- Turn on the operating voltage and set it to 15 V.
- Set the function generator to a sinusoidal signal with $f = 50$ Hz and bring it to the input.
- Observe the input voltage (U_E) and output voltage (U_A) with the oscilloscope.
- Magnify the input signal's amplitude at the function generator as long as the output signal is still sinusoidal.
- Determine the effective voltages $U_{\text{eff}} = \frac{1}{\sqrt{2}} \frac{U_{SS}}{2}$ at the input and output (open-circuit voltage) using the oscilloscope.
- Measure the input amperage with the multimeter.
- Short-circuit the output and measure its amperage (short circuit current).
- Connect the load resistor 10 kΩ to the output; determine the output voltage and amperage.
- Calculate the powers and the amplification factors according to (1).

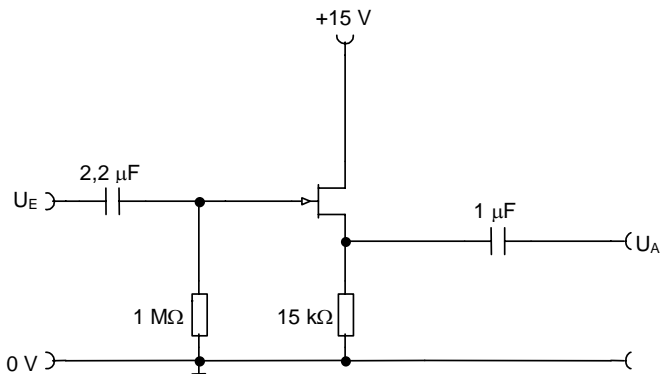b) Field-effect transistor in common drain



- Repeat the experiment according to a).
- Calculate the amperage with $I_{E,\text{eff}} = \frac{U_{E,\text{eff}}}{1 \text{ M}\Omega}$.

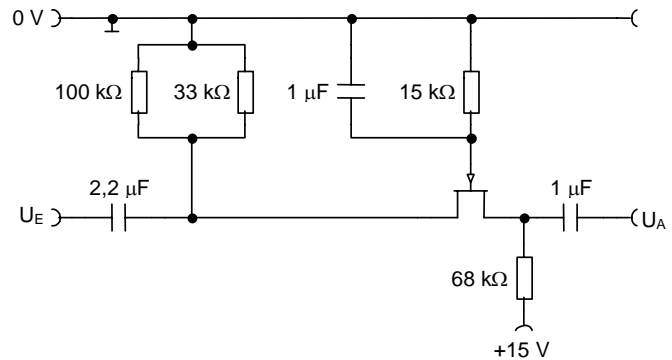c) Field-effect transistor in common gate




- Repeat the experiment according to a).

Note: The experiments should also be conducted with other frequencies.

Measurement Examples

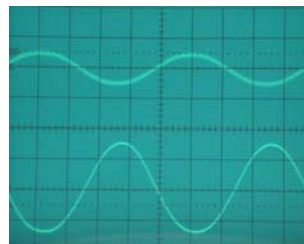a) Field-effect transistor in common source

Note: In each of the oscilloscope images, the input voltage is represented on top and the output voltage on the bottom.




Y I: 50 mV/div AC
 Y II: 0.5 V/div AC
 Sweep: 5 msec/div

Input E		
Voltage	$U_{E,\text{eff}}$	28 mV
Amperage	$I_{E,\text{eff}}$	2 μA
Power	P_E	0.056 μW
Output A		
Idle	$U_{A,\text{eff}}$	350 mV
	V_U	12.5
Short circuit	$I_{A,\text{eff}}$	11 μA
	V_I	5.5
Charge with 10 kΩ	$U_{A,\text{eff}}$	106 mV
	$I_{A,\text{eff}}$	9 μA
	P_A	0.95 μW
	V_U	3.8
	V_I	4.5
	$V_U \cdot V_I$	17


- The power amplification factor is produced by the product of the amperage's and the voltage's amplification factors:
 $V_P \approx V_U \cdot V_I$

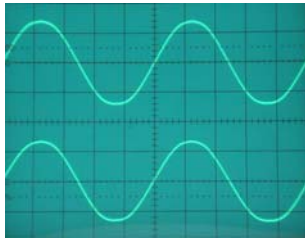b) Field-effect transistor in common drain



Y I: 0.2 V/div AC
 Y II: 0.2 V/div AC
 Sweep: 5 msec/div

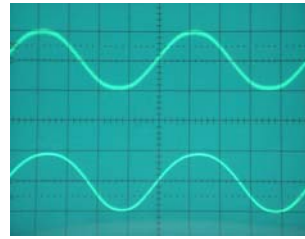c) Field-effect transistor in common gate



Y I: 50 mV/div AC
 Y II: 1 V/div AC
 Sweep: 5 msec/div

Input E		
Voltage	$U_{E,eff}$	180 mV
Amperage	$I_{E,eff}$	0.18 μ A
Power	P_E	0.03 μ W
Output A		
Idle	$U_{A,eff}$	180 mV
	V_U	1
Short circuit	$I_{A,eff}$	44 μ A
	V_I	240
Charge with 10 k Ω	$U_{A,eff}$	155 mV
	$I_{A,eff}$	15 μ A
	P_A	2.3 μ W
	V_U	0.9
	V_I	83
	V_P	77
	$V_U \cdot V_I$	75

Input E		
Voltage	$U_{E,eff}$	35 mV
Amperage	$I_{E,eff}$	12.5 μ A
Power	P_E	0.44 μ W
Output A		
Idle	$U_{A,eff}$	670 mV
	V_U	19
Short circuit	$I_{A,eff}$	14 μ A
	V_I	1.1
Charge with 10 k Ω	$U_{A,eff}$	120 mV
	$I_{A,eff}$	12 μ A
	P_A	1.44 μ W
	V_U	3.4
	V_I	0.96
	V_P	3.3
	$V_U \cdot V_I$	3.3

- The voltage amplification factor is about 1 (no voltage amplification): $V_U \approx 1$
- Therefore the power amplification factor matches that of the amperage: $V_P \approx V_I$
- The amperage amplification is large.

- The amperage amplification factor is about 1 (no amperage amplification): $V_I \approx 1$
- Therefore the power amplification factor matches that of the voltage: $V_P \approx V_U$

